


# High Frequency Technologies

## Problems on transmission lines

---
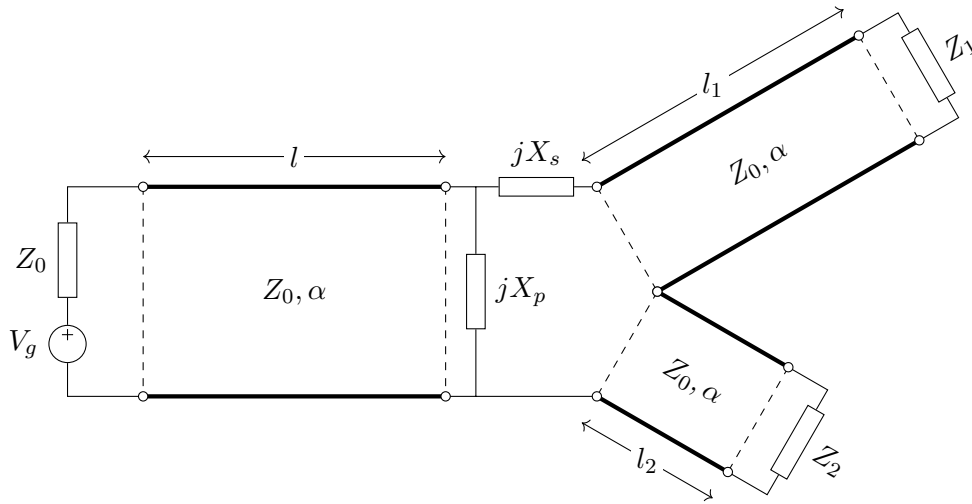
### Problem 1

We want to feed two antennas with input impedances  $Z_1 = 40\ \Omega$  and  $Z_2 = 60\ \Omega$ , with a generator of peak voltage  $V_g = 10\text{ V}$ , frequency  $f_0 = 2\text{ GHz}$ , and internal impedance  $Z_0 = 50\ \Omega$ . To do so, a lossless three-port network will be used, with an equivalent circuit shown in the figure (the part composed of the reactances  $jX_p$  and  $jX_s$ ). The three-port network is connected to the other elements through coaxial cables with characteristic impedance  $Z_0$ . The length of the cable that connects the common port and the generator is  $\beta l = \frac{3\pi}{4}$  rad, while the antenna cables that connect the other ports with the loads  $Z_1$  and  $Z_2$  have lengths  $\beta l_1 = \frac{\pi}{2}$  rad and  $\beta l_2 = \pi$  rad, respectively. Find the power delivered to each antenna.



**Note** The coaxial cable attenuation is  $3.5 \times 10^{-3}\text{ Np/cm}$ . The matching network reactances are  $X_s = 10\ \Omega$  and  $X_p = 100\ \Omega$ .

**Answer**

$$P_1 = 86.129\text{ mW}, P_2 = 80.239\text{ mW}.$$

### Problem 2

A shunt resistance  $R = 100\ \Omega$  is connected at an arbitrary point between the two conductors of a lossless transmission line with characteristic impedance  $Z_0 = 50\ \Omega$ . One of the transmission line ends is connected to a generator with internal impedance  $Z_0$  and available power  $P_{\text{av}} = 250\text{ mW}$ , while the other end is loaded with  $Z_0$ . Determine:

- The incident and reflected voltage and current waves between the generator and the  $100\ \Omega$  resistor, and also between the resistor and the load.

- b) The power dissipated in the resistor, the power delivered to the load, and also the power reflected to the generator.

### Answer

- Power reflected to the generator: 10 mW
- Power delivered to the load: 160 mW
- Power dissipated in  $R$ : 80 mW

### Problem 3

Find the ratio between the maximum power that can be transmitted in a lossless transmission line when its load is matched ( $P_1$ ), and the transmitted power when there is an arbitrary standing wave ratio  $S$  ( $P_2$ ). Suppose that the only limitation is the electric breakdown, so that the maximum electric field strength supported by the dielectric is  $E_{\text{rup}}$ .

### Answer


$$\frac{P_1}{P_2} = \text{SWR}$$

### Problem 4

Using the computer, characterize the electrical parameters along a transmission line terminated with loads corresponding to different reflection coefficient values  $\Gamma_L$ . Try this five loads: short circuit, open circuit, pure inductance, pure capacitance, and a complex load with inductive character. Draw both the voltage and current waves, as well as the reflection coefficient. Do it for different time instants.
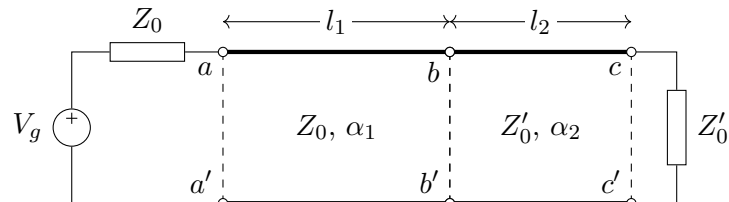
### Problem 5

Consider the following network, composed of two sections of transmission line, with a source and a load.



Find:

- The power  $P_a$ , delivered at the input of the first transmission line section ( $a/a'$ ).
- The power  $P_b$ , delivered at the input of the second transmission line section ( $b/b'$ ).

- c) The power  $P_c$ , delivered to the load ( $c/c'$ ).
- d) If  $\alpha_1 = \alpha_2 = 0$  (lossless transmission lines), sketch the envelope of the voltage along the transmission line sections.


**Answer**

a)  $P_a = \frac{|V_g|^2}{8Z_0} \left( 1 - \left| \frac{Z'_0 - Z_0}{Z'_0 + Z_0} \right|^2 e^{-4\alpha_1 l_1} \right)$

b)  $P_b = \frac{|V_g|^2}{8Z_0} \left( 1 - \left| \frac{Z'_0 - Z_0}{Z'_0 + Z_0} \right|^2 \right) e^{-2\alpha_1 l_1}$


c)  $P_c = \frac{|V_g|^2}{8Z_0} \left( 1 - \left| \frac{Z'_0 - Z_0}{Z'_0 + Z_0} \right|^2 \right) e^{-2(\alpha_1 l_1 + \alpha_2 l_2)}$

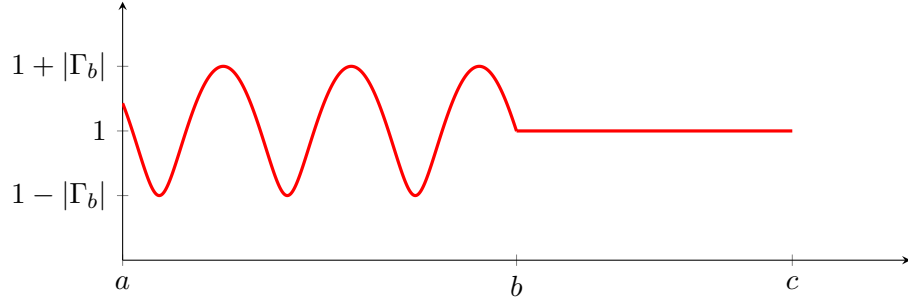d) Voltage envelope (with  $\Gamma_b = \frac{Z'_0 - Z_0}{Z'_0 + Z_0}$ ):


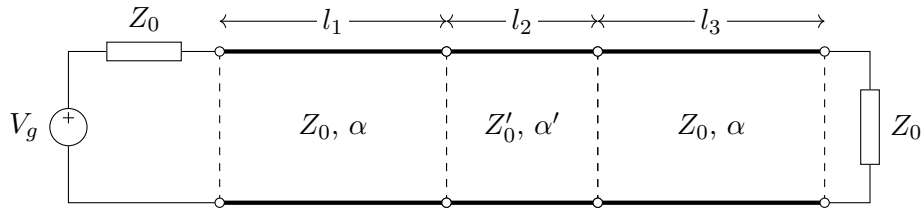
## Problem 6

Compute the power delivered to the load  $Z_L = Z_0$  from the source with frequency 1 GHz, peak voltage  $V_g = 10$  V, and internal impedance  $Z_0$ , when they are connected by three cascaded sections of transmission lines, as shown in the schematic,



where the dielectric of the transmission lines has  $\epsilon_r = 1$ , their lengths are  $l_1 = 2$  m,  $l_2 = 10$  cm,  $l_3 = 1$  m, and their respective characteristic impedances and attenuations are:

- First and third sections:  $Z_0 = 50 \Omega$ ,  $\alpha = 3.5 \times 10^{-3}$  Np/cm.
- Second section:  $Z'_0 = 75 \Omega$ ,  $\alpha' = 3 \times 10^{-3}$  Np/cm.

## Answer

The power delivered to the load is

$$P_L = P_{av} \frac{(1 - |\Gamma_{1o}|^2)(1 - |\Gamma_{2o}|^2)(1 - |\Gamma_{3o}|^2)}{(1 - |\Gamma_{2i}|^2)(1 - |\Gamma_{3i}|^2)} e^{-2(\alpha l_1 + \alpha' l_2 + \alpha l_3)} = 25.57 \text{ mW}$$

where  $\Gamma_{ki}$  and  $\Gamma_{ko}$  are, respectively, the reflection coefficients seen at the input and output of the  $k^{\text{th}}$  transmission line section,

$$\begin{aligned}\Gamma_{1i} &= 0.0814 e^{-2.5687j} & \Gamma_{1o} &= 0.3300 e^{-0.474j} \\ \Gamma_{2i} &= 0.1884 e^{-1.047j} & \Gamma_{2o} &= -0.2 \\ \Gamma_{3i} &= 0 & \Gamma_{3o} &= 0\end{aligned}$$

and  $P_{av} = 250 \text{ mW}$  is the available power of the source.